


Presentador: Victor Miguel Barrera Peña

Tema: 10 Multiplexor

Teoría

Hay que recordar como es electrónicamente, existe.


Esquema funcionamiento

 

Del lado izquierdo vemos como se ve en VHDL, del lado derecho vemos como físicamente se movería.


Diferentes tamaños

 Si vieramos diferentes tamaños de multiplexor, podría ser como las siguientes :



¿Qué es lo que hace?

 Cambia entre los diferentes canales de entrada de acuerdo a los bits asignados del selector.



s_1	s_2	e (hex)	Salida (Hex)
0	0	A	A
0	1	B	B
1	0	C	C
1	1	D	D

Veamos el código

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity p10 is  
    port(  
        entrada : in std_logic_vector(3 downto 0);  
        selector : in std_logic_vector (1 downto 0);  
        salida: out std_logic  
    );  
end entity p10;
```

```
architecture behavior of p10 is begin
```

```
    with selector select
```

```
        salida <= entrada(0) when "00",
```

```
        entrada(1) when "01",
```

```
        entrada(2) when "10",
```

```
        entrada(3) when others;
```

```
end architecture behavior;
```

Veamos su comportamiento



**Muchas
gracias
por ver el
video**